

1.

s_1	s_2	s_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


2. Sum-of-Products expression:

$$f(s_1, s_2, s_3) = \bar{s}_1 \bar{s}_2 s_3 + \bar{s}_1 s_2 \bar{s}_3 + s_1 \bar{s}_2 s_3 + s_1 s_2 s_3 = \sum (1, 2, 4, 7)$$

3. Product-of-Sums expression:

$$f(s_1, s_2, s_3) = (s_1 + s_2 + s_3) \cdot (s_1 + \bar{s}_2 + \bar{s}_3) \cdot (\bar{s}_1 + s_2 + \bar{s}_3) \cdot (\bar{s}_1 + \bar{s}_2 + s_3) \\ = \prod (0, 3, 5, 6)$$


4. Logic Diagram:

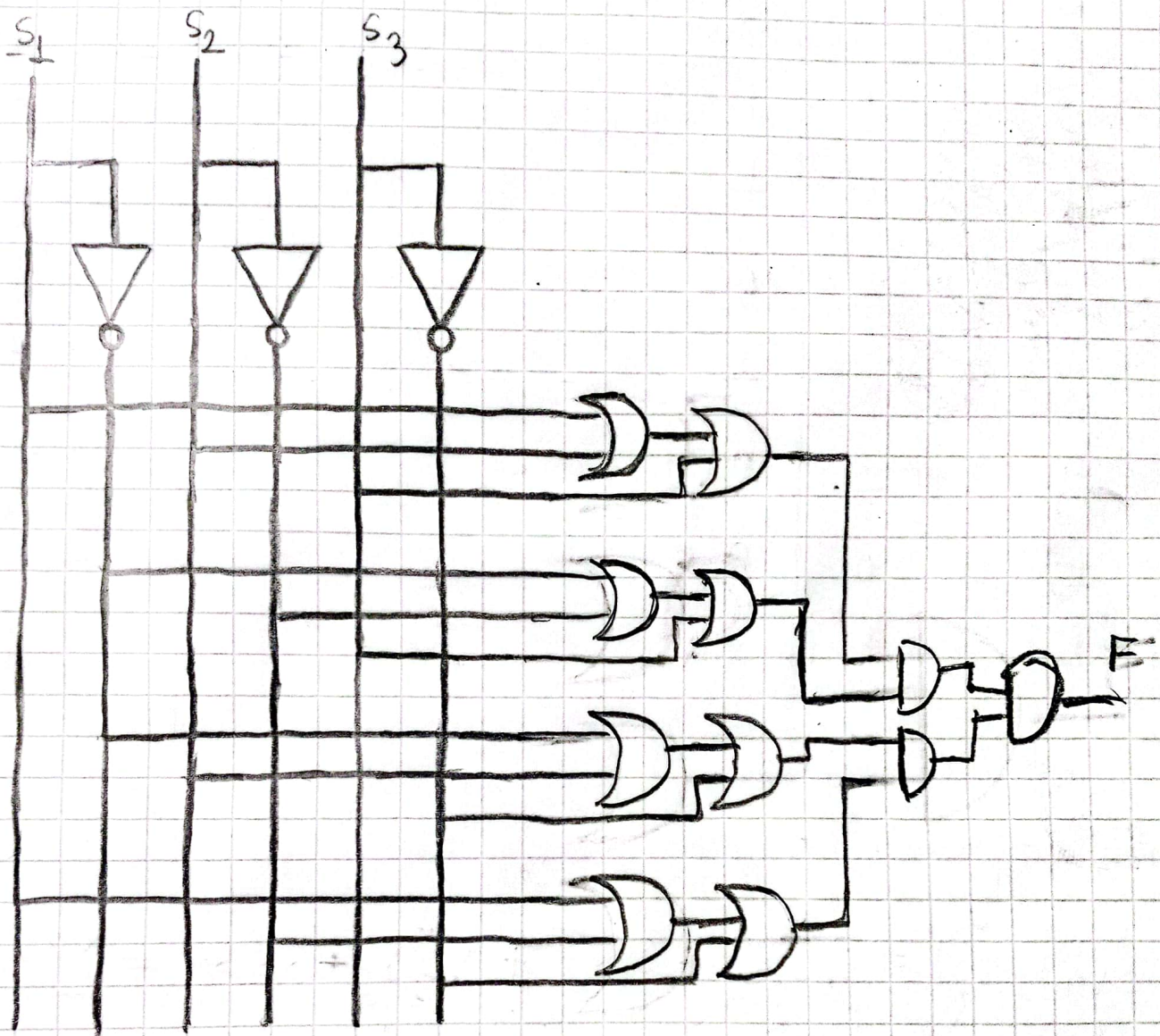

- a) One 74LS08 Quad 2 input AND gate
 - b) Two 74LS32 Quad 2-input OR gate
 - c) One 74LS04 Hex INV gate
- } Integrated Circuits

* In this logic diagram; 3 INV, 8 OR, 3 AND gates are planned to use.

6. Circuit Schematic:

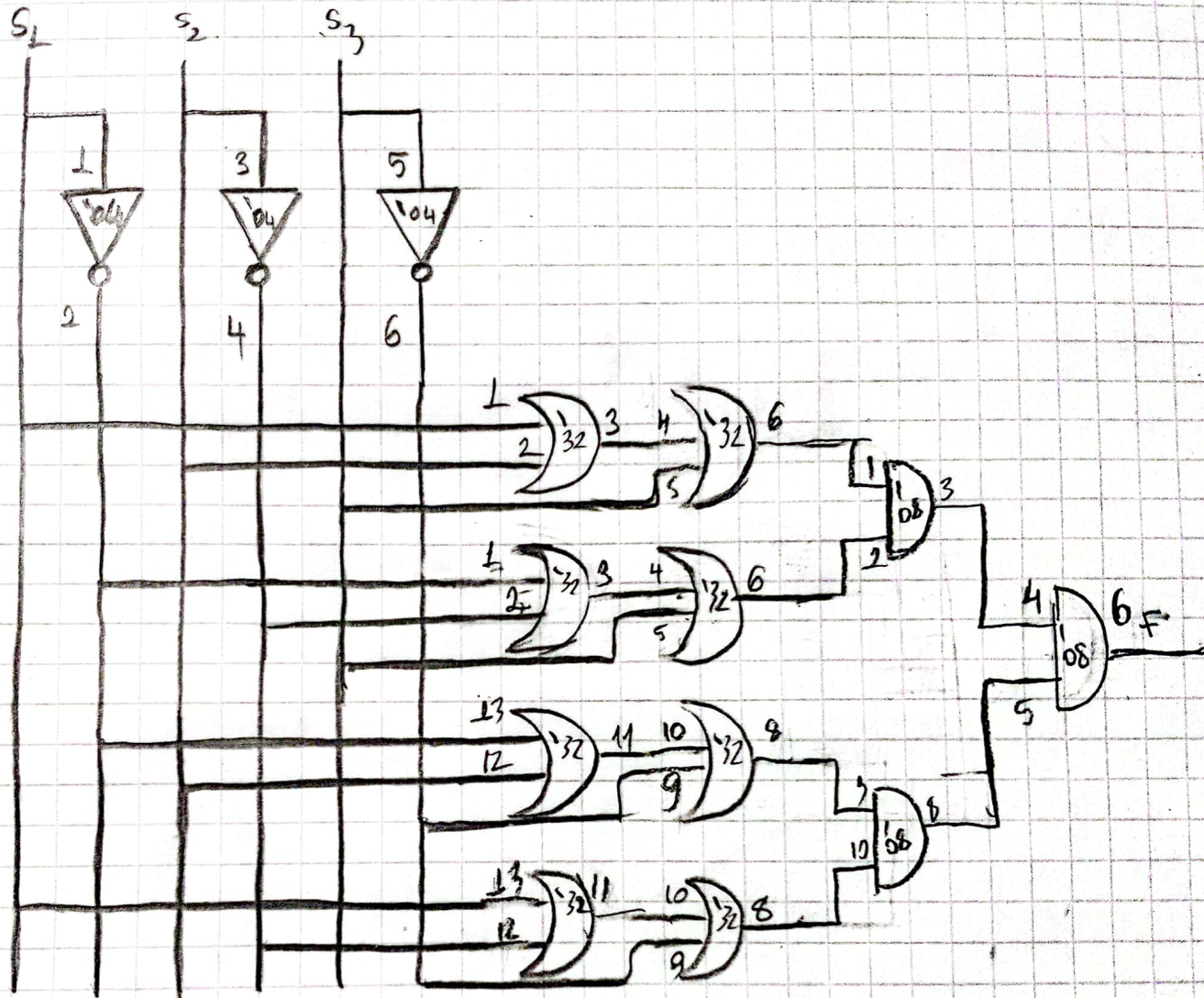

• 74LS08 → GND-7
+5V-14

• 74LS32 → GND-7
+5V-14

• 74LS04 → GND-7
+5V-14